 



### 4-bit Carry Save Adder

$$S = \sum_{i=1}^k w_i$$



### 4-bit CSA-CLA

$$S = \sum_{i=1}^k w_i$$

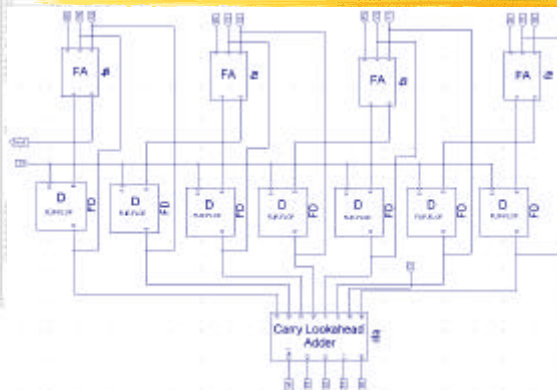

### Multiplication

- ✦ Multiplication of an  $m$ -bit number  $X$  by and  $n$ -bit number  $Y$
- ✦  $M > N$
- ✦ To yield  $Z = X \cdot Y$  with  $m+n$  bits
- ✦ This may be accomplished by forming  $n$  partial products  $P_i$  where:

$$P_i = Y_i \cdot X$$

- ✦ This requires  $m$  AND gates

### 4-Bit Partial Products

$$Z = P_0 + 2 \cdot P_1 + 2^2 \cdot P_2 + 2^3 \cdot P_3$$




## Partial Products

⊕ We then weight each  $P_i$  with  $2^i$  and sum them:

$$Z = P_0 + 2 \cdot P_1 + 2^2 \cdot P_2 + \dots + 2^{n-1} \cdot P_{n-1}$$

⊕ For example if  $m=56$  and  $n=8$  we use a Wallace tree of six CSAs to reduce 8 partial products to 2 which are completed by a single Carry Lookahead Adder.

## Wallace Tree Multiplier

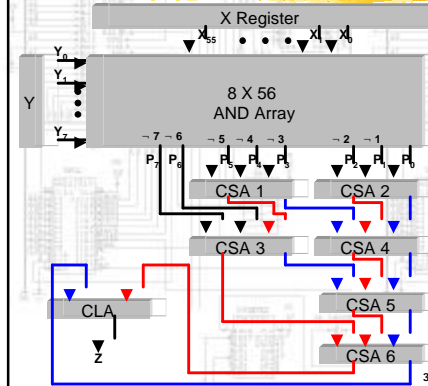

⊕ The CSA range from 58-63 bits wide.  
⊕ The CLA is 64 bits wide

## Shift and Add Multiplication


23	10111	Multiplicand
19	10011	Multiplier
	10111	← $P_0$
	10111	← $P_1 \cdot 2^1$
	00000	← $P_2 \cdot 2^2$
	00000	← $P_3 \cdot 2^3$
	10111	← $P_4 \cdot 2^4$
437	110110101	Product

## Hardware Multiplication

23	10111	Multiplicand
19	10011	Multiplier
	00000	Initial partial product
	10111	Add multiplicand, since multiplier bit is 1
	10111	Partial product after add and before shift
	010111	Partial product after shift
	10111	Add multiplicand, since multiplier bit is 1
	1000101	Partial product after add and before shift <sup>a</sup>
	1000101	Partial product after shift
	01000101	Partial product after shift
	001000101	Partial product after shift
	10111	Add multiplicand, since multiplier bit is 1
	110110101	Partial product after add and before shift
437	0110110101	Product after final shift

▶ a. Overflow temporarily occurred

## 3BA5 Binary Multiplier Diagram

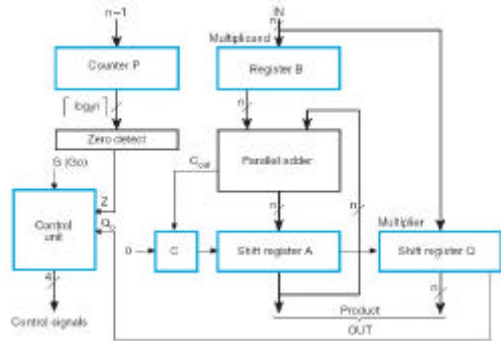

3BA5, 13<sup>th</sup> Lecture, M. Manzke, Page: 9

## 3BA5 Booth's Algorithm

- ⊕ This effectively halves the number of partial products in a multiplication.
- ⊕ Principle:

$$Z = X * Y$$

$$X = 00111\dots100$$

$$X = 2^{k+1} - 2^j$$

3BA5, 13<sup>th</sup> Lecture, M. Manzke, Page: 10

## 3BA5 Booth's Algorithm

$k-j+1$

- ⊕ We may replace the  $k-j+1$  non-zero partial products with just two:

$$\begin{aligned} P_1 &= 2^{k+1} * Y \\ P_2 &= -2^j * Y \\ Z &= P_1 + P_2 \end{aligned}$$

3BA5, 13<sup>th</sup> Lecture, M. Manzke, Page: 11

## 3BA5 Booth's Algorithm

Worst case

- ⊕ Of course in general a multiplier will have more than one such sequence of consecutive ONES.
- ⊕ The most extrem case is that of alternating zero and one.
- ⊕ Resulting in  $n/2$

$$\text{Worst case} = 010101010101$$

3BA5, 13<sup>th</sup> Lecture, M. Manzke, Page: 12

## Booth's Algorithm

### Sequences of three bits

✦ Thus to detect and generate all the appropriate partial products we examine overlapping sequences of three bits:

$X_{i+1}, X_i$   
Bits examined

$X_{i-1}$   
Previously Examined Bit