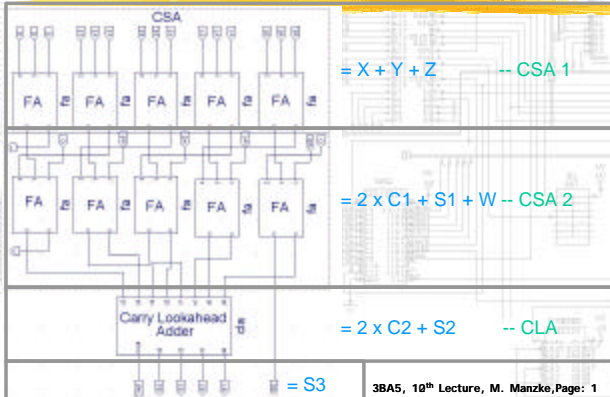


3BA5

4-bit CSA/CLA Block Diagram

$$S = X + Y + Z + W$$

3BA5, 10th Lecture, M. Manzke, Page: 1**3BA5**

4-bit CSA/CLA VHDL Code

$$X + Y + Z \text{ -- CSA} \quad [\text{entity CSA}]$$

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity CSA is
  Port ( X : in std_logic_vector(4 downto 0);
        Y : in std_logic_vector(4 downto 0);
        C_in : in std_logic_vector(4 downto 0);
        S : out std_logic_vector(4 downto 0);
        C_out : out std_logic_vector(4 downto 0));
end CSA;
architecture structural of CSA is
  COMPONENT fa
    PORT ( X : IN std_logic;
          Y : IN std_logic;
          C_in : IN std_logic;
          S : OUT std_logic;
          C_out : OUT std_logic);
  END COMPONENT;

```

3BA5, 12th Lecture, M. Manzke, Page: 2**3BA5**

4-bit CSA/CLA VHDL Code

$$X + Y + Z \text{ -- CSA} \quad [\text{begin}]$$

```

begin
fa_0: fa PORT MAP(X => X(0),
                 Y => Y(0),
                 C_in => C_in(0),
                 S => S(0),
                 C_out => C_out(0));

fa_1: fa PORT MAP(X => X(1),
                 Y => Y(1),
                 C_in => C_in(1),
                 S => S(1),
                 C_out => C_out(1));

fa_2: fa PORT MAP(X => X(2),
                 Y => Y(2),
                 C_in => C_in(2),
                 S => S(2),
                 C_out => C_out(2));

```

3BA5, 12th Lecture, M. Manzke, Page: 3**3BA5**

4-bit CSA/CLA VHDL Code

$$X + Y + Z \text{ -- CSA} \quad [\text{end structural}]$$

```

fa_3: fa PORT MAP(X => X(3),
                 Y => Y(3),
                 C_in => C_in(3),
                 S => S(3),
                 C_out => C_out(3));

fa_4: fa PORT MAP(X => X(4),
                 Y => Y(4),
                 C_in => C_in(4),
                 S => S(4),
                 C_out => C_out(4));

end structural;

```

3BA5, 12th Lecture, M. Manzke, Page: 4

3BA5

4-bit CSA/CLA VHDL Code

 $2 \times C1 + S1 + W \text{ -- FA}$ []

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity FA is
  Port ( X : in std_logic;
        Y : in std_logic;
        C_in : in std_logic;
        S : out std_logic;
        C_out : out std_logic);
end FA;
architecture concurrent_behavior of FA is
  signal S1, S2, S3 : std_logic;
begin
  S1 <= (X xor Y);
  S2 <= (c_in and S1);
  S3 <= (X and Y);
  S <= (S1 xor C_in);
  C_out <= (S2 xor S3);
end concurrent_behavior;

```

3BA5, 12th Lecture, M. Manzke, Page: 5**3BA5**

4-bit CSA/CLA VHDL Code

 $2 \times C2 + S2 \text{ -- CLA}$ [entity CLA]

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity CLA is
  Port ( X : in std_logic_vector(3 downto 0);
        Y : in std_logic_vector(3 downto 0);
        S : out std_logic_vector(3 downto 0);
        C_out : out std_logic);
end CLA;
architecture concurrent_behavior of CLA is
  signal p0, p1, p2, p3, g0, g1, g2, g3 : std_logic;
  signal c0p0 : std_logic;
  signal p1g0, p1p0c0 : std_logic;
  signal p2g1, p2p1g0, p2p1p0c0 : std_logic;
  signal p3g2, p3p2g1, p3p2p1g0, p3p2p1p0c0 : std_logic;
  signal c1, c2, c3 : std_logic;
  signal c0 : std_logic := '0';

```

3BA5, 12th Lecture, M. Manzke, Page: 6**3BA5**

4-bit CSA/CLA VHDL Code

 $2 \times C2 + S2 \text{ -- CLA}$ [begin]

```

begin
  p0 <= (X(0) or Y(0));
  p1 <= (X(1) or Y(1));
  p2 <= (X(2) or Y(2));
  p3 <= (X(3) or Y(3));
  g0 <= (X(0) and Y(0));
  g1 <= (X(1) and Y(1));
  g2 <= (X(2) and Y(2));
  g3 <= (X(3) and Y(3));

  c0p0 <= (p0 and c0);
  c1 <= (g0 or c0p0);

  p1g0 <= (p1 and g0);
  p1p0c0 <= (p1 and p0 and c0);
  c2 <= (g1 or p1g0 or p1p0c0);

```

3BA5, 12th Lecture, M. Manzke, Page: 7**3BA5**

4-bit CSA/CLA VHDL Code

 $2 \times C2 + S2 \text{ -- CLA}$ [end concurrent_behavior]

```

  p2g1 <= (p2 and g1);
  p2p1g0 <= (p2 and p1 and g0);
  p2p1p0c0 <= (p2 and p1 and p0 and c0);
  c3 <= (g2 or p2g1 or p2p1g0 or p2p1p0c0);

  p3g2 <= (p3 and g2);
  p3p2g1 <= (p3 and p2 and g1);
  p3p2p1g0 <= (p3 and p2 and p1 and g0);
  p3p2p1p0c0 <= (p3 and p2 and p1 and p0 and c0);
  C_out <= (g3 or p3g2 or p3p2g1 or p3p2p1g0 or p3p2p1p0c0);

  S(0) <= (X(0) xor Y(0) xor c0);
  S(1) <= (X(1) xor Y(1) xor c1);
  S(2) <= (X(2) xor Y(2) xor c2);
  S(3) <= (X(3) xor Y(3) xor c3);
end concurrent_behavior;

```

3BA5, 12th Lecture, M. Manzke, Page: 8

3BA5

4-bit CSA/CLA VHDL Code

 $S3 = X + Y + Z + W$ [entity XYZW_ADDER]

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity XYZW_ADDER is
  Port ( X : in std_logic_vector(3 downto 0);
        Y : in std_logic_vector(3 downto 0);
        Z : in std_logic_vector(3 downto 0);
        W : in std_logic_vector(3 downto 0);
        S : out std_logic_vector(4 downto 0);
        C_out : out std_logic);
end XYZW_ADDER;

```

3BA5

4-bit CSA/CLA VHDL Code

 $S3 = X + Y + Z + W$ [COMPONENT csa/cla]

```

architecture structural of XYZW_ADDER is
  COMPONENT csa
    PORT(
      X : IN std_logic_vector(4 downto 0);
      Y : IN std_logic_vector(4 downto 0);
      C_in : IN std_logic_vector(4 downto 0);
      S : OUT std_logic_vector(4 downto 0);
      C_out : OUT std_logic_vector(4 downto 0));
  END COMPONENT;
  COMPONENT cla
    PORT(
      X : IN std_logic_vector(3 downto 0);
      Y : IN std_logic_vector(3 downto 0);
      S : OUT std_logic_vector(3 downto 0);
      C_out : OUT std_logic);
  END COMPONENT;

```

3BA5

4-bit CSA/CLA VHDL Code

 $S3 = X + Y + Z + W$ [signal]

```

-- signal that connect the input ports with the CSAs
signal X_in, Y_in, Z_in, W_in : std_logic_vector(4 downto 0);

-- signal that connect the 1st CSA with the 2nd CSA
signal S_01, C_out_01 : std_logic_vector(4 downto 0);

-- signal that connect the 2nd CSA with the CLA
signal S_CSA_2, C_out_12, C_out_01S : std_logic_vector(4 downto 0);

begin
  X_in <= ('0' & X);
  Y_in <= ('0' & Y);
  Z_in <= ('0' & Z);
  W_in <= ('0' & W);
  C_out_01S <= (C_out_01(3 downto 0) & '0');
  S(0) <= S_CSA_2(0);

```

3BA5

4-bit CSA/CLA VHDL Code

 $S3 = X + Y + Z + W$ [PORT MAP]

```

Inst0_csa: csa PORT MAP(
  X => X_in,
  Y => Y_in,
  C_in => Z_in,
  S => S_01,
  C_out => C_out_01);

Inst1_csa: csa PORT MAP(
  X => S_01,
  Y => W_in,
  C_in => C_out_01S,
  S => S_CSA_2,
  C_out => C_out_12);

Inst0_cla: cla PORT MAP(
  X => S_CSA_2(4 downto 1),
  Y => C_out_12(3 downto 0),
  S => S(4 downto 1),
  C_out => C_out);

end structural;

```

Repeated Summation

$$S = \sum_{i=1}^k w_i$$

⊕ Procedure

```
X ? 0, Y ? 0;           // Initialise
do i = 1 to k
  Z ? Wi;
  X ? Sum(X + 2Y + Z);  // CSA
  Y ? Carry(X + 2Y + Z);
end;
S ? X + 2Y;           // CLA
```